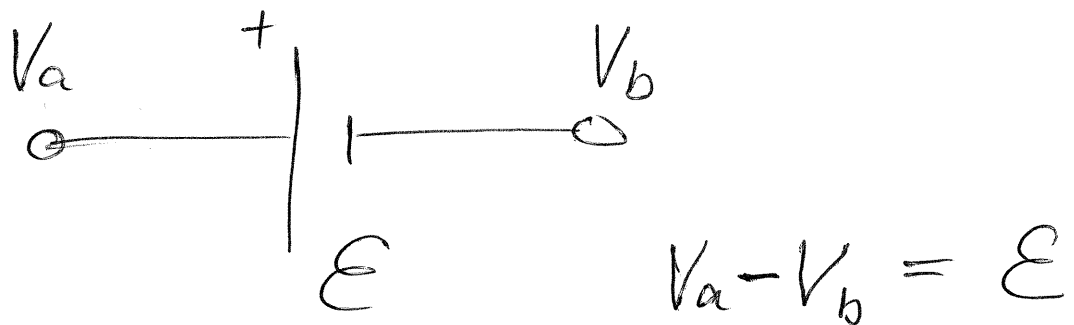


# Lecture 16


(1)

In circuit theory the icon for a "pure emf" is



where  $E$  is the energy per unit charge ~~to~~ acquired by charges as they move from terminal **b** to terminal **a** (the side indicated by "+"). An actual battery will also have internal resistance in addition to the pure emf

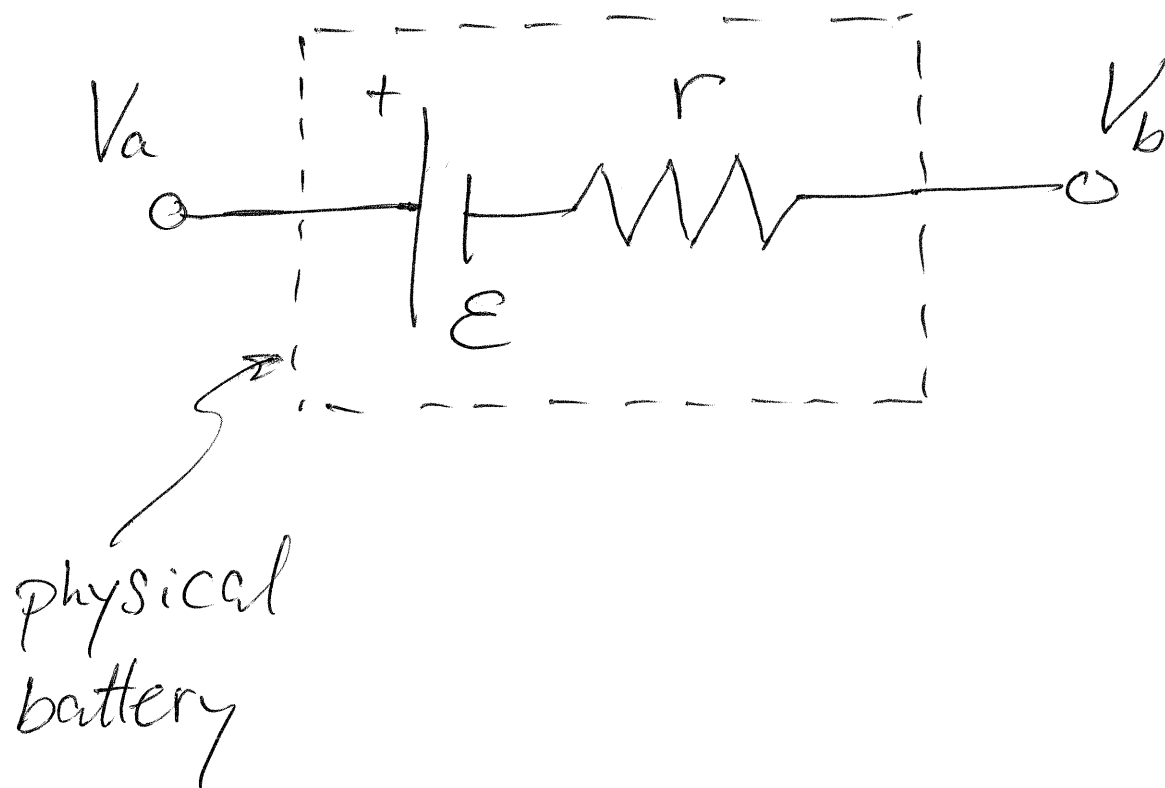
derived from chemical reactions. Both elements are represented schematically like this: (2)



The potential  $V_a - V_b$  across the terminals of the battery now also depends on the amount of current  $I$  flowing through the

3

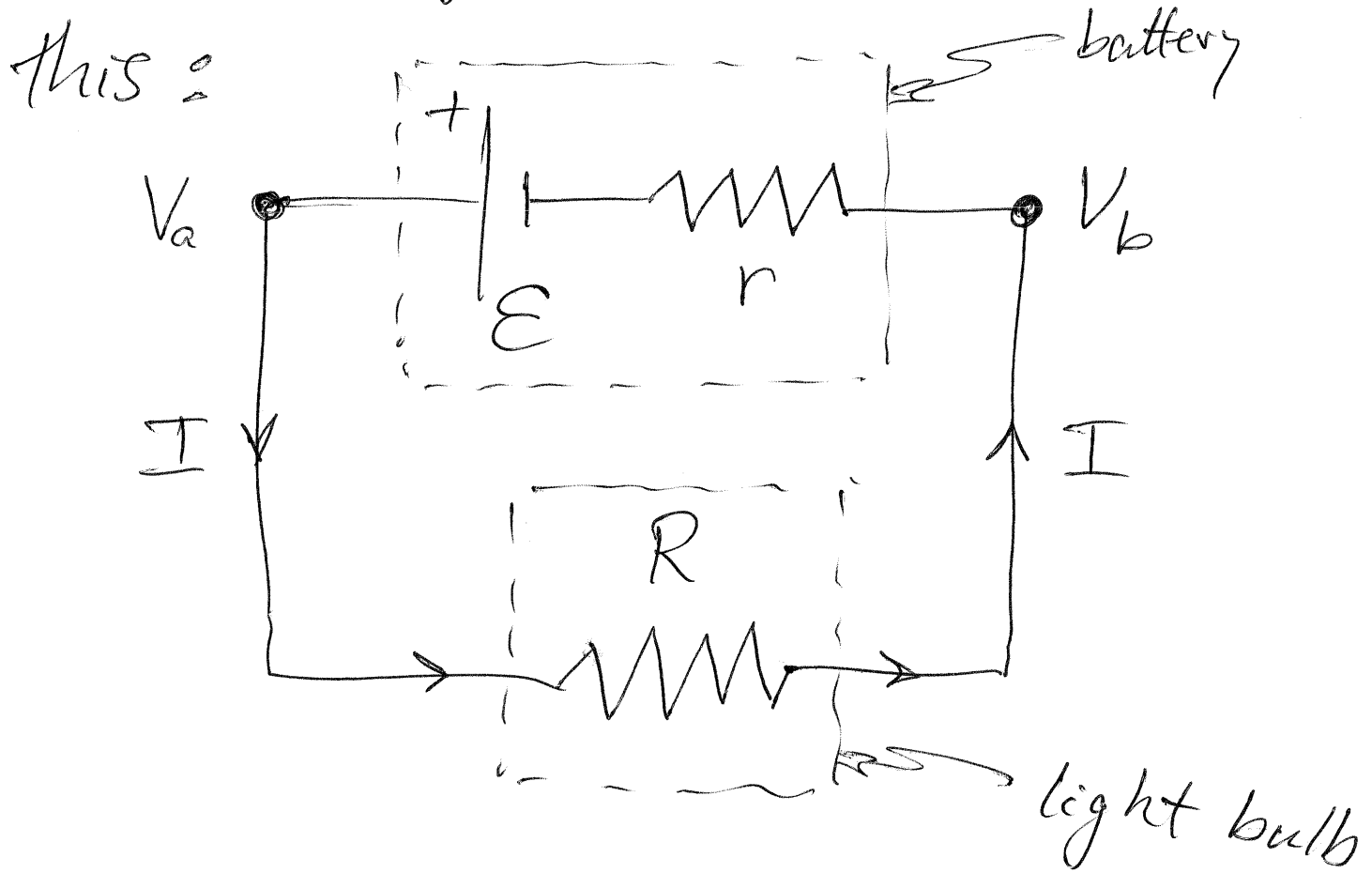battery, since all of this current flows through the internal resistance  $r$  which has its own, current dependent, voltage difference. Attaching the battery to a light bulb we get a "complete" circuit like



The light bulb is represented <sup>(4)</sup>  
as a resistor  $R$ , since its  
action on the flow of charge  
is no different. In a light bulb  
the electrical energy is dissipated  
in a very small amount of  
material — a thin filament —  
so that it becomes very hot  
and emits radiation (electro-  
magnetic waves, actually!). The  
strong temperature variation of  
light bulbs has the effect that  
 $R$  is not as constant as it is  
in proper resistors.


We can relate the quantities (5)  
in our circuit diagram by  
invoking two principles of  
physics:

(I) charge conservation

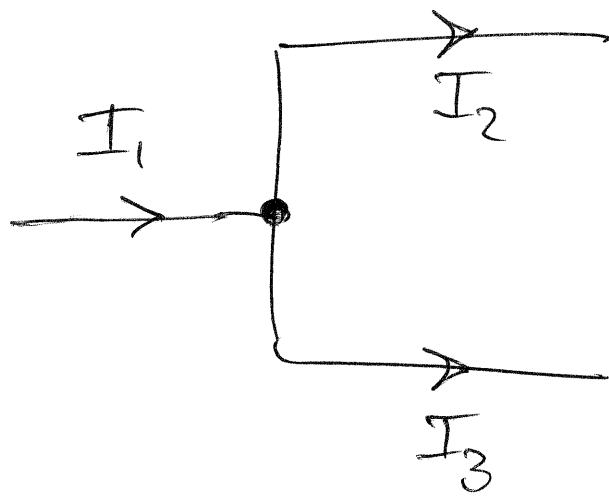(II) energy conservation

Principle (I) is satisfied simply  
by the fact that we were care-  
ful to ensure that the same  
current  $I$  is flowing into and  
out of any component. If this  
were not the case, then by

conservation of charge there <sup>(6)</sup> would be an accumulation of positive or negative charge in the battery or light bulb and we would not have a steady-state. Later, when we study capacitors there will be charge accumulations and non-steady currents. Junctions involving three or more currents are also possible and are dealt with by imposing constraints on the sums of currents :



$$I_1 = I_2 + I_3$$

Principle (I) is called Kirchhoff's "junction rule" in electrical engineering.

Principle (II) asserts that when a charge is moved in the direction of the current around a loop in the circuit its energy is unchanged. The circuit is in a sense a model of a closed system, where all sources and

losses of energy are accounted (8)  
for. In our battery + light-bulb  
loop, for example, the current  
flow is counter-clockwise and  
a charge  $q$  gains energy  $+ \mathcal{E}q$   
moving through the battery and  
~~loses~~ loses energy  $-V_r q$  and  
 $-V_R q$  moving through the two  
resistors. The resistor voltages  
are current-dependent:

$$V_r = Ir \quad , \quad V_R = IR$$

Setting the net energy change  
equal to zero we find:



$$\begin{aligned} \mathcal{E} &= I_r + IR \\ &= I(r+R) \end{aligned}$$

9

More generally (say we have several loops in our circuit) principle II asserts that it is possible to consistently assign a unique voltage to all the terminals, and for that to be true the voltages around any loop must sum to zero.

Electrical engineers call this Kirchhoff's "loop rule".

Notice that the voltage

across the physical battery (10)  
 $V = V_a - V_b$  is not the same  
as the "chemical" emf,  $\mathcal{E}$ . In  
fact, the voltage  $V$  is exactly  
the voltage across the bulb  
when a current  $I$  is flowing  
through its resistance  $R$ :

$$V = V_a - V_b = \text{battery terminal voltage}$$

$$V = IR$$

$$= \left( \frac{\mathcal{E}}{r+R} \right) R = \left( \frac{R}{R+r} \right) \mathcal{E} < \mathcal{E}$$

The actual voltage applied to  
the bulb,  $V$ , will be significantly


reduced relative to  $\mathcal{E}$  when (11)  
the internal resistance  $r$  of  
the battery is large.

The conservation of energy  
principle has an ~~close~~ equivalent  
expression in terms of power.

We will illustrate this using the  
example of a circuit that  
shows a weak battery being  
"charged" by a stronger battery.

Note that "charging" is a poor  
choice of verb in that the battery  
remains charge neutral while actually  
receiving energy/power.

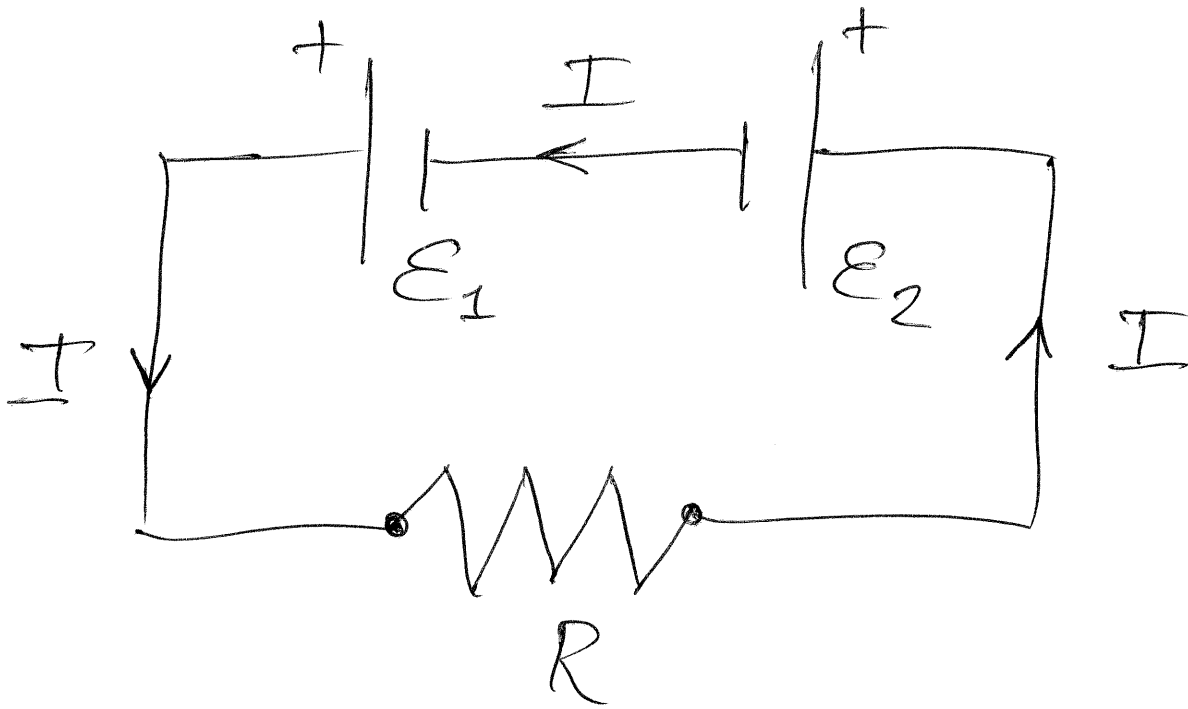We will omit explicit internal resistances to keep things simple: (12)



loop rule:  $\mathcal{E}_1 - \mathcal{E}_2 - IR = 0$

$\mathcal{E}_1 > \mathcal{E}_2 \Rightarrow I > 0$

$\mathcal{E}_1 = \mathcal{E}_2 + IR$  mult. by  $I$

$\mathcal{E}_1 I = \mathcal{E}_2 I + I^2 R$

(13)

The last equation is a power equation. It states that the power output of the strong battery (1) equals the ~~the~~ power input to the weak battery (2) and the loss of power in the resistor.



Q: the weak battery gains power because current is flowing through it in the "wrong" direction. Describe the mechanism of energy gain in the case of a lead-acid battery.