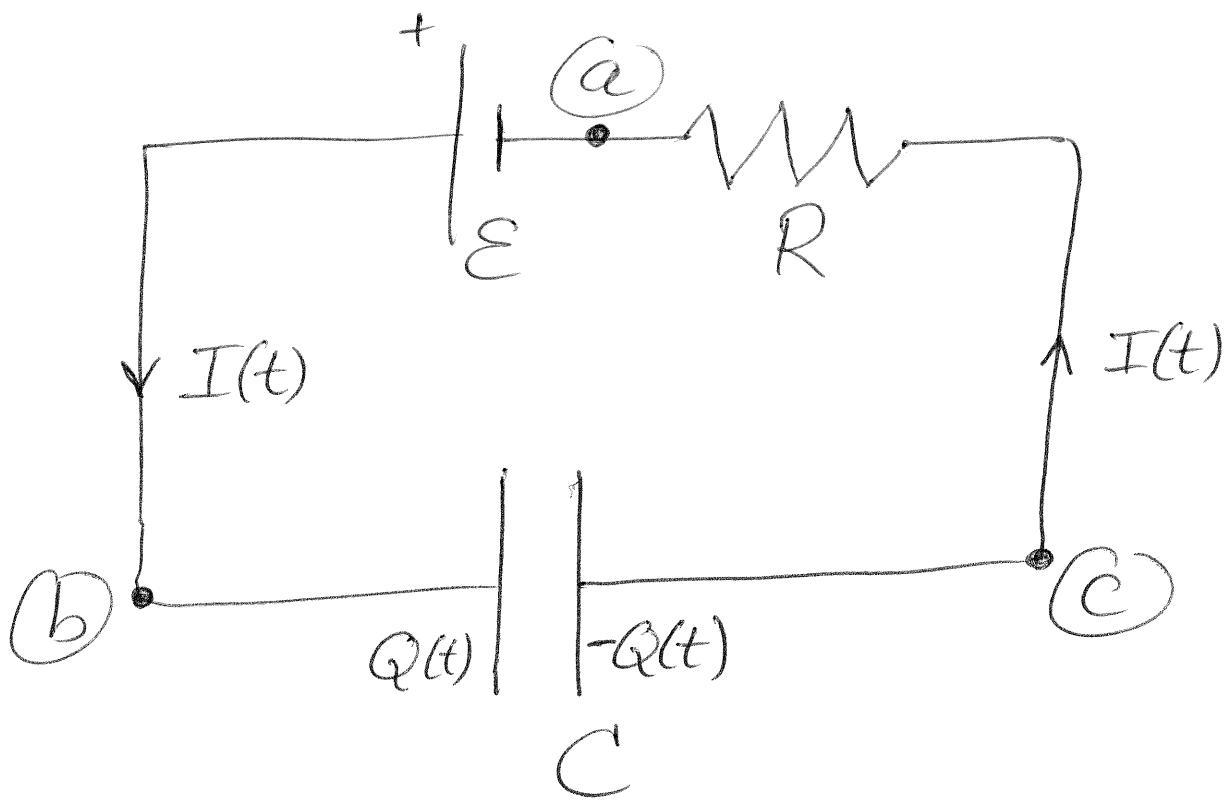


①

## Lecture 19

Let's apply the "loop rule" to the capacitor charging circuit:



The pure emf raises the potential by  $+\mathcal{E}$  as we go from  $\textcircled{A}$  to  $\textcircled{B}$ .  
 The voltage across the capacitor

is  $V = \frac{Q(t)}{C}$  (definition of ②  
the capacitance  $C$ ) where higher  
potential terminal is the one  
with positive charge (since  $\vec{E}$   
is directed from the positive plate  
to the negative plate). Therefore,  
if  $Q(t) > 0$  in the diagram, the  
potential will drop by  $-\frac{Q(t)}{C}$   
as we go from ⑥ to ⑦. This  
change in potential is also correct  
if  $Q(t) < 0$ ; in that case the  
potential increases (the direction  
of  $\vec{E}$  is reversed) and  $-\frac{Q(t)}{C}$  is  
a potential rise (positive quantity).

Finally, in going from C ~~to~~ (3) back to A through the resistor the potential drops by  $-IR$  (if it turned out that  $I$  was negative the potential in the resistor would drop when moving in the opposite direction — it always drops when moving in the direction of positive current). The three potential changes must bring us back to the original potential:

$$\text{loop rule: } +E - \frac{Q(t)}{C} - I(t)R = 0$$

This equation contains two unknowns:  $Q(t)$  and  $I(t)$ . We

need another equation that relates these unknowns. What's needed is the statement of charge conservation applied to the individual plates of the capacitor:

$$\frac{dQ(t)}{dt} = I(t) \quad (\text{left plate})$$

If this is satisfied then

$$\frac{d(-Q(t))}{dt} = -I(t) \quad (\text{right plate})$$

is also true and we have charge conservation ~~on~~ on both plates.

Substituting  $\dot{Q}$  for  $I$  in the (5) loop equation we get the following differential equation:

$$E - Q/C - \dot{Q}R = 0$$

The corresponding homogeneous equation ( $E \rightarrow 0$ ) is

$$\dot{Q}_h = -\frac{1}{RC} Q_h$$

with general solution

$$Q_h(t) = Q_h(0) e^{-t/RC}$$

A particular solution of the

loop equation is

⑥

$$Q(t) = CE \quad (= \text{const.})$$

The most general solution is then this solution plus the most general solution of the homogeneous equation:

$$Q(t) = CE + Q_h(0)e^{-t/RC}$$

Different choices of the constant  $Q_h(0)$  correspond to different scenarios or initial conditions.

If initially ~~at~~ ( $t=0$ ) the capacitor is uncharged, then we


$$\text{want } Q_h(0) = -CE \quad : \quad (7)$$

charging solution:

$$Q(t) = CE(1 - e^{-t/\tau})$$

$\tau = RC$  = "time constant"

Ohm  $\times$  Farad = second

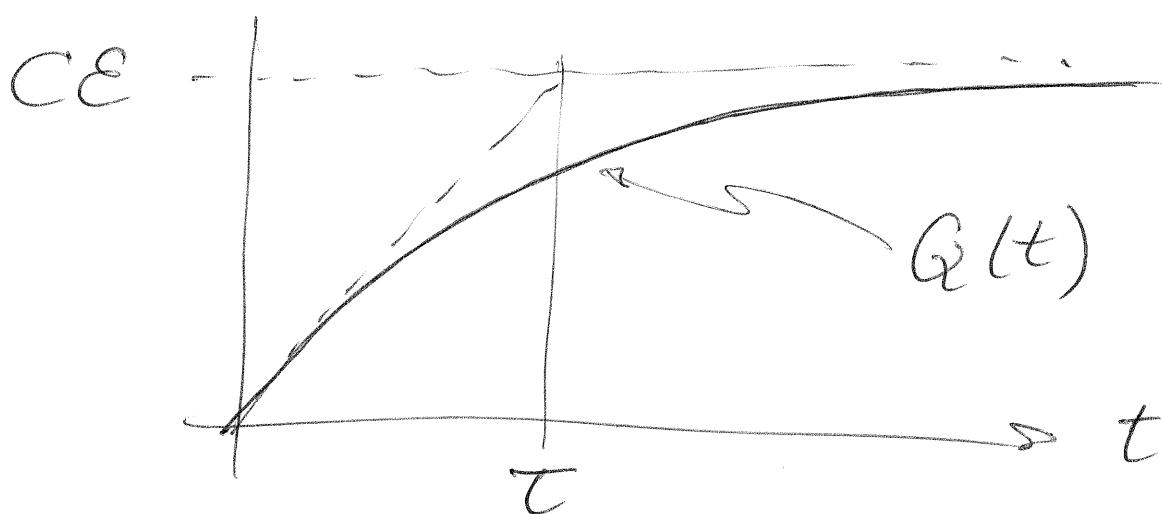

The charge approaches the static equilibrium ( $I=0$ ) value

$Q = CE$  on an exponentially diminishing asymptote. A straight-line extrapolation of the initial slope,

$$I(0) = \dot{Q}(0) = \frac{CE}{\tau}$$

would reach  $Q = CE$  in the time  $\tau$ .

+—————,

A "charged" or energized capacitor can be directly connected to a circuit without a battery and will drive a current. Our circuit diagram for charging

still applies if we set  $\epsilon = 0$  (no battery) and interpret the resistance as the device (light-bulb, etc.) we are driving.

The equation is then

$$\dot{Q} = -\frac{1}{\tau} Q ,$$

with general solution :

$$Q(t) = Q(0) e^{-t/\tau} \quad \text{"discharging"}$$

