
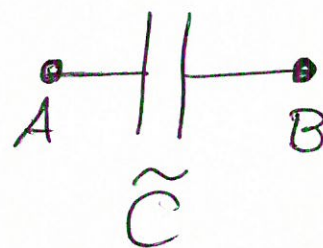


# Assignment 7 Solutions

(1)

infinite square grid of capacitors

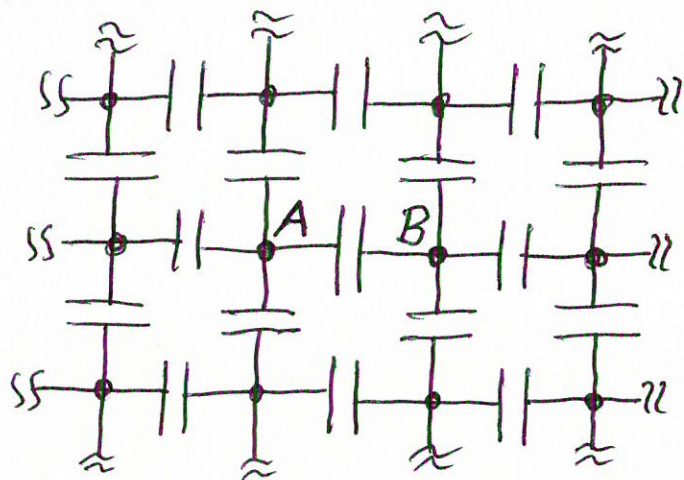


all capacitors have


$$C = 1F$$

If  $+Q$  is placed on node A, and  $-Q$  on node B, and  $\Phi_A - \Phi_B = V$ , then the infinite grid behaves like a single capacitor  $\tilde{C}$  with capacitance  $Q/V$ . We will work out this ratio using symmetry.

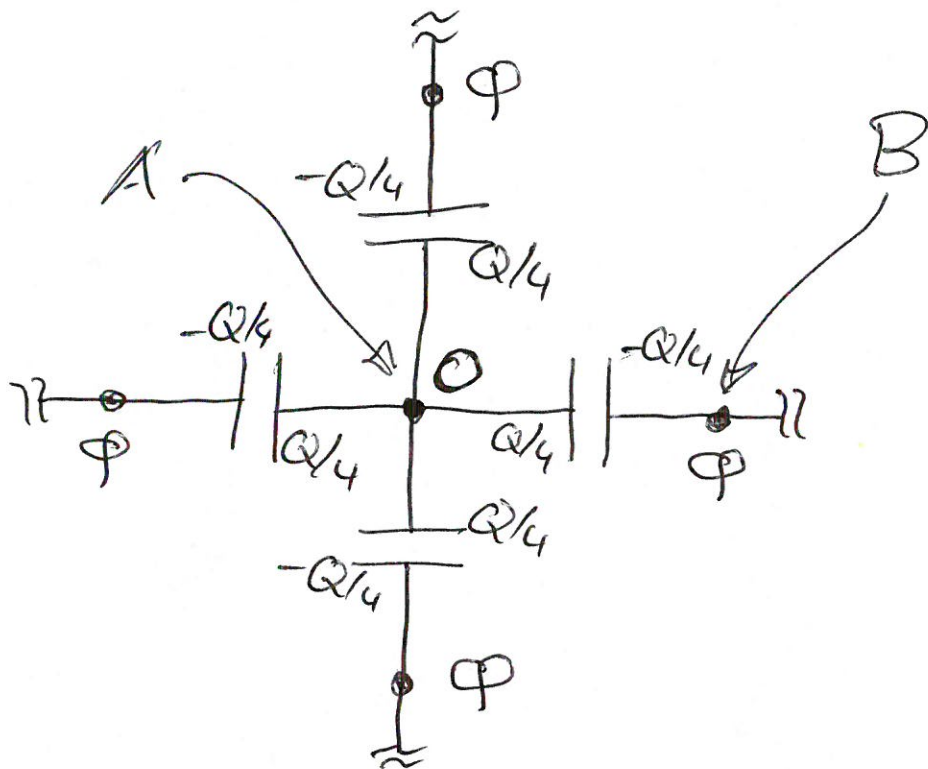When just  $+Q$  is placed at A,  $(\Sigma)$   
 and we set  $\Phi_A = 0$ , we get the  
 following charge/potential arrangement  
 near A:




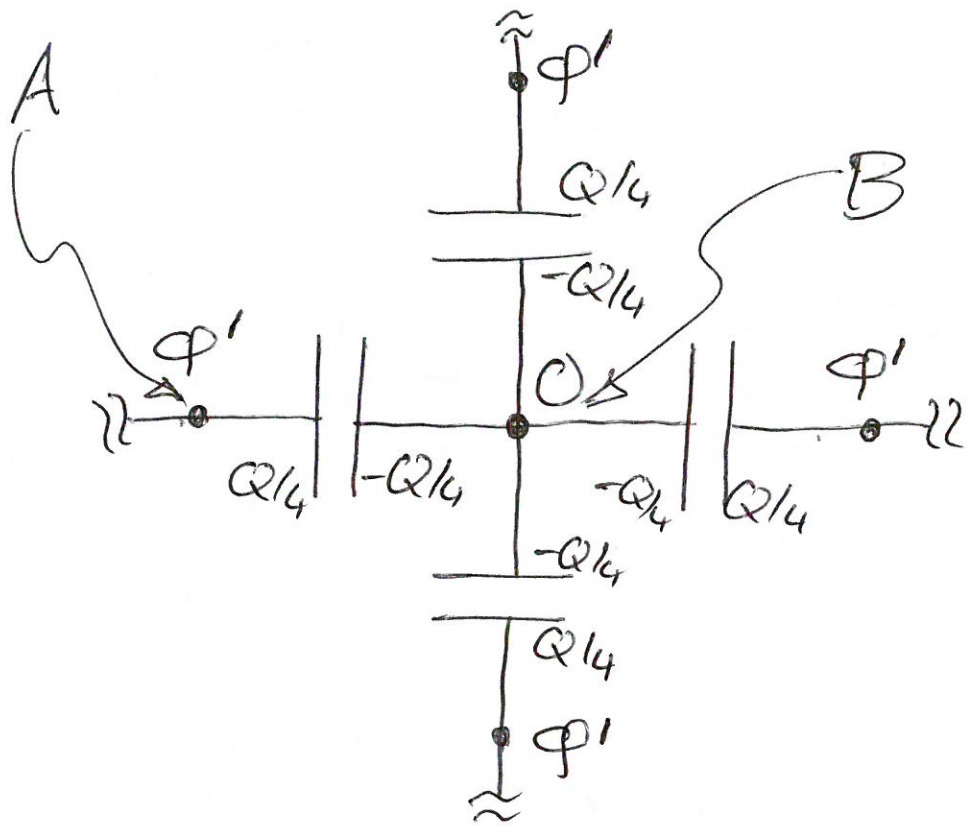Where  $\Phi = \frac{-Q/4}{C}$  on the four  
 nodes adjacent to A. Now, make  
 a similar drawing symmetric  
 about B, but with charge  $-Q$   
 at that node (next page).



$\phi' = \frac{+Q/4}{C}$ . Now superpose the

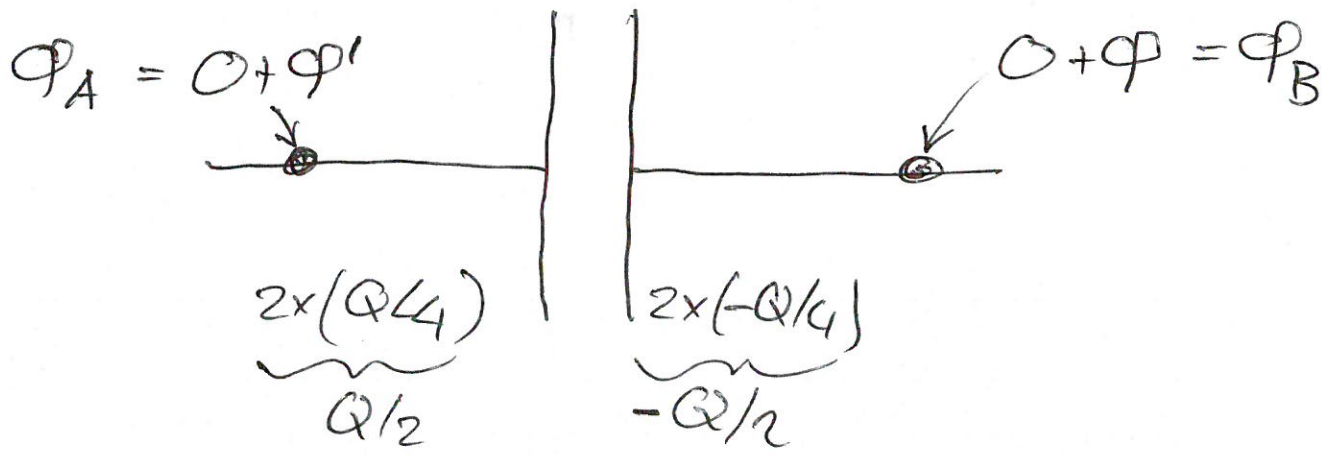two drawings, focusing on nodes A, B and the charge on the capacitor between them:






In the superposition, charge  $+Q$  (4) is placed on node A, and charge  $-Q$  is placed on node B, as asked in the problem.

$$V = \Phi_A - \Phi_B = \Phi' - \Phi = \frac{Q}{4C} - \left(\frac{-Q}{4C}\right) = \frac{Q}{2C}$$

From this we see that

$$\tilde{C} = Q/V = 2C = 2F.$$

Energy/power in simple RC circuit

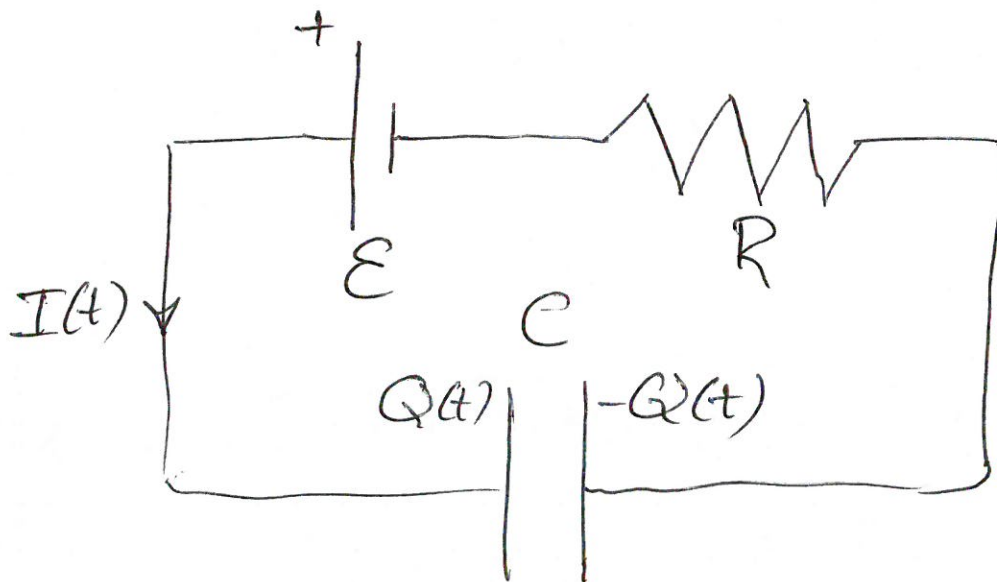

At  $t=0$   $Q=0$ , so the potential <sup>(5)</sup> across the capacitor is  $Q/C = 0$ , the loop rule simplifies to

$$\mathcal{E} - I(0)R = 0$$

$$\Rightarrow I(0) = \mathcal{E}/R$$

At  $t = \infty$   $I = 0$ , so there is no potential drop at the resistor, ~~and~~ the loop rule again simplifies:

$$\mathcal{E} - \frac{Q(\infty)}{C} = 0$$

$$\Rightarrow Q(\infty) = \mathcal{E}C$$

---

From lecture,  $Q(t) = \mathcal{E}C(1 - e^{-t/\tau})$

$$\tau = RC$$

power provided by EMF:

⑥

$$\begin{aligned} \mathcal{E}I(t) &= \mathcal{E}\dot{Q} = \mathcal{E} \frac{\mathcal{E}C}{\tau} e^{-t/\tau} \\ &= \frac{\mathcal{E}^2}{R} e^{-t/\tau} \end{aligned}$$

power consumed by (stored in) the capacitor:

$$\begin{aligned} \frac{d}{dt} \left( \frac{1}{2} \frac{Q^2(t)}{C} \right) &= \frac{Q}{C} \dot{Q} = \mathcal{E} (1 - e^{-t/\tau}) \frac{\mathcal{E}}{R} e^{-t/\tau} \\ &= \frac{\mathcal{E}^2}{R} (e^{-t/\tau} - e^{-2t/\tau}) \end{aligned}$$

power dissipated by resistor:

$$RI^2 = \frac{\mathcal{E}^2}{R} e^{-2t/\tau}$$

---

$$\frac{\mathcal{E}^2}{R} \left( \underbrace{+e^{-t/\tau}}_{\text{EMF}} - \underbrace{(e^{-t/\tau} - e^{-2t/\tau})}_{\text{capacitor}} - \underbrace{e^{-2t/\tau}}_{\text{resistor}} \right) = 0$$

total energy provided by EMF: (7)

$$\int_0^{\infty} \frac{\mathcal{E}^2}{R} e^{-t/\tau} dt = \frac{\mathcal{E}^2}{R} (-\tau) e^{-t/\tau} \Big|_0^{\infty}$$
$$= \frac{\mathcal{E}^2}{R} \tau = \mathcal{E}^2 C$$

final energy stored in capacitor:

$$\frac{1}{2} C V(\infty)^2 = \frac{1}{2} C \mathcal{E}^2$$

From this we see that energy

$$\mathcal{E}^2 C - \frac{1}{2} \mathcal{E}^2 C = \frac{1}{2} \mathcal{E}^2 C$$

was dissipated (lost to heat) in the resistor.